


Name: \_\_\_\_\_

Date: \_\_\_\_\_


Period: \_\_\_\_\_

## Equivalent Resistance

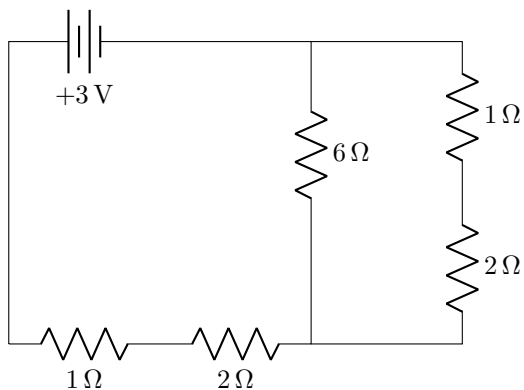1. **Consolidation:** Find the current going through the battery in the circuit below.



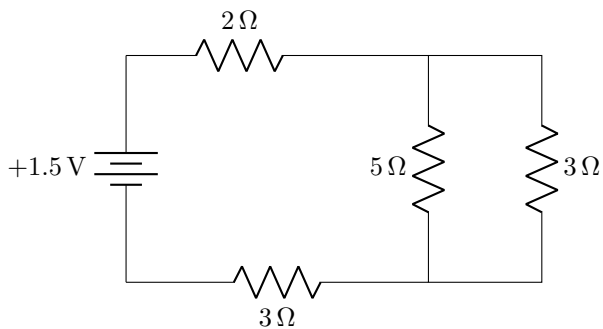2. Find the current going through the battery in the circuit below.




Name: \_\_\_\_\_


Date: \_\_\_\_\_

Period: \_\_\_\_\_

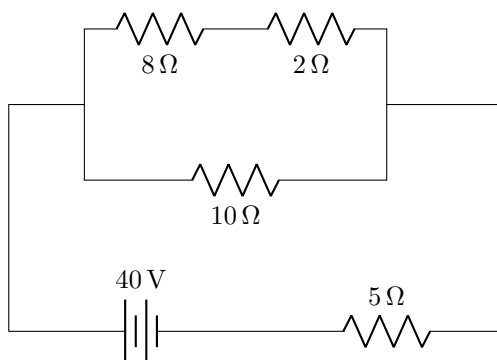3. Find the current going through the battery in the circuit below.



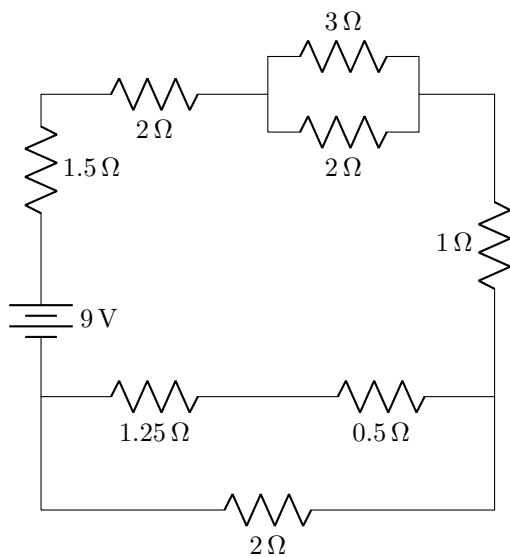4. Find the current going through the battery in the circuit below.




Answers:      3) 4.00 A      4) 1.49 A

Name: \_\_\_\_\_

Date: \_\_\_\_\_

Period: \_\_\_\_\_

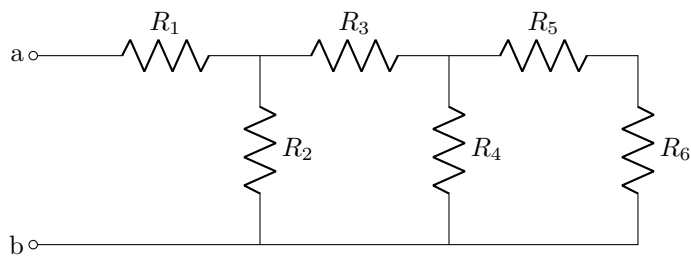5. Consider the following circuit, in which  $R_1 = R_3 = R_5 = R_6 = 1\text{ k}\Omega$  and  $R_2 = R_4 = 2\text{ k}\Omega$ .



- (a) Calculate Equivalent Resistance
- (b) A 9-volt battery is connected between points  $a$  and  $b$ . Calculate the current through *each* resistor.
- (c) Calculate the potential difference across each resistor.

Name: \_\_\_\_\_

Date: \_\_\_\_\_

Period: \_\_\_\_\_

6. **Bonus:** Calculate the equivalent resistance of a cube that has a 1-ohm resistor along each edge.

