





Name: _____

Date: _____

Period: _____

Series vs. Parallel Lab

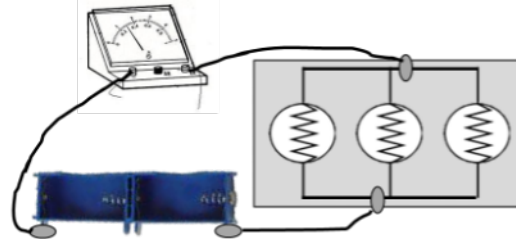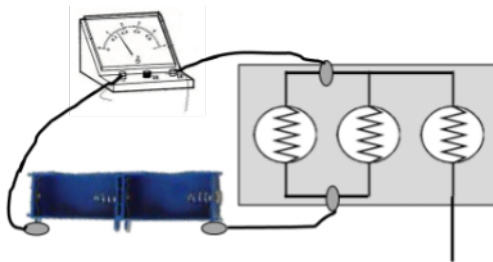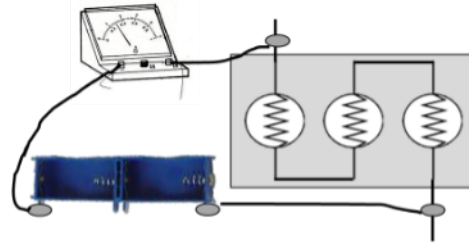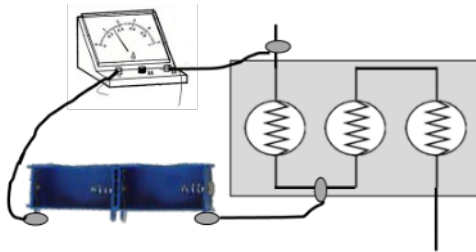1. Study the circuits below and describe whether they are series or parallel and how many bulbs will light up.



2. What will be your independent and dependent variables in this lab?
3. **Purpose:** Write one or two sentences explaining what you are trying to figure out in this lab. Make sure your purpose includes all of your independent and dependent variables
4. **Hypothesis:** What do you predict will happen to the current through the battery as more light bulbs are added in series and parallel?

Name:

Date:

Period:

5. **Data:** Show all data tables for each of your experiments.

Current Through a Series Circuit

# of bulbs	current (amps)
1	
2	
3	

Current Through a Parallel Circuit

# of bulbs	current (amps)
1	
2	
3	

6. Create two scatter plots for your data

Current Through a Series Circuit



Current Through a Parallel Circuit



7. **Results:** What was the relationship between your independent variable and your dependent variable (*i.e.* directly proportional, inversely proportional, no effect, unclear) for each setup? Did they match your hypothesis?
8. **Conclusions:** What happens when more bulbs are added in series? In parallel? Why does this make sense?