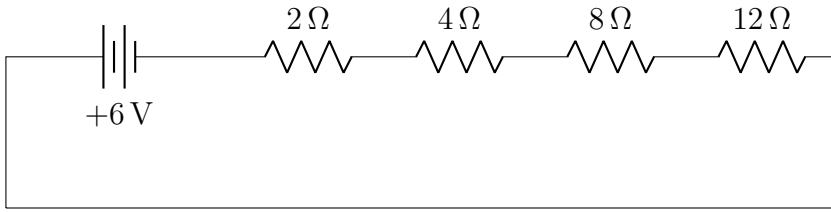
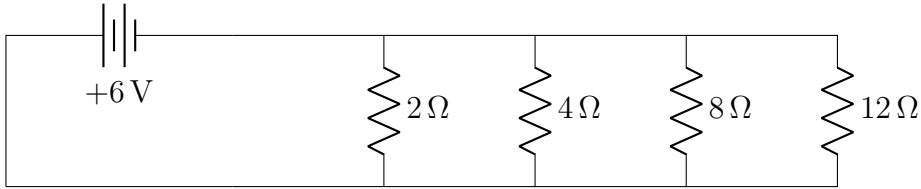

Task #1

Find the current going through the battery in each of the circuits below:

(a)

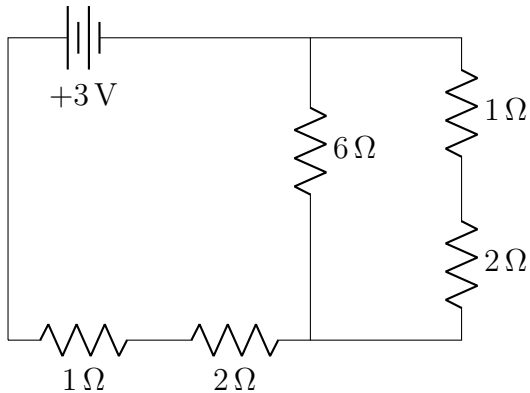


(b)



Task #2

Find the current going through the battery in the circuit below.



Task #3

Find the current going through the battery in the circuit below.

