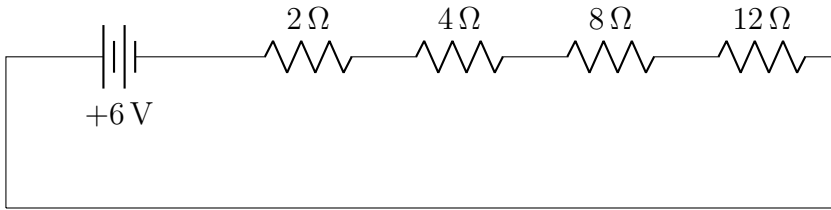


---


**Task #1**

Find the current going through the battery in each of the circuits below:

(a)




(b)

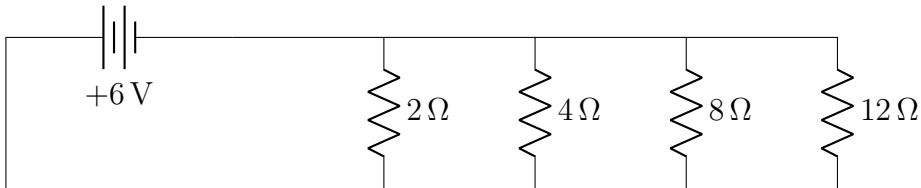

---

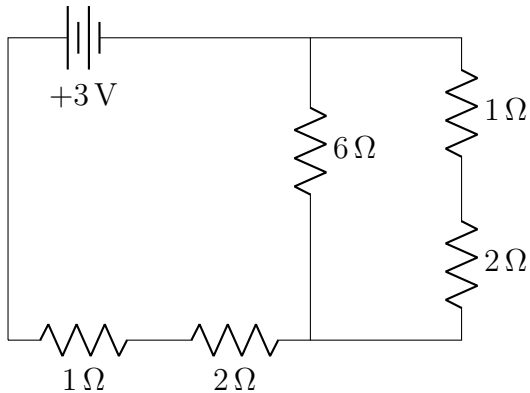**Task #2**


Find the current going through the battery in the circuit below.



---

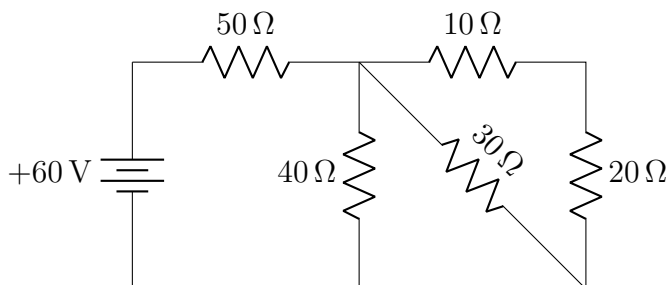**Task #3**

Find the current going through the battery in the circuit below.



---

Task #1

(a)  $R_{eq} = 26 \text{ ohm}$ ;  $I = 0.221 \text{ Amps}$ .

(b)  $R_{eq} = \frac{24}{23} = 1.04 \text{ ohm}$ ;  $I = 5.75 \text{ Amps}$ .

Task #2

$R_{eq} = 5 \text{ ohm}$ ;  $I = 0.6 \text{ Amps}$ .

Task #3

$R = 60.9 \text{ ohm}$ ;  $I = 0.99 \text{ Amps}$ .

---