


Name: _____

Date: _____


Period: _____

Equivalent Resistance

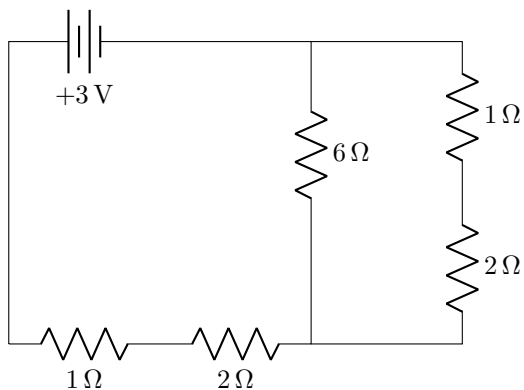1. **Consolidation:** Find the current going through the battery in the circuit below.



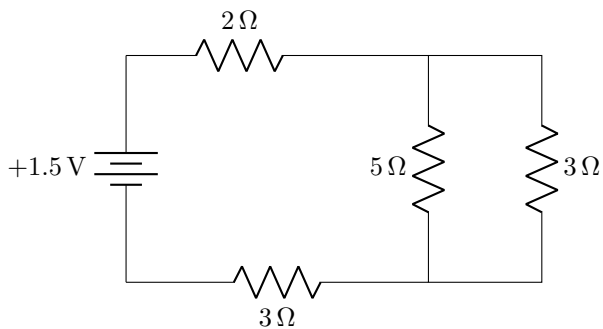2. Find the current going through the battery in the circuit below.




Name: _____


Date: _____

Period: _____

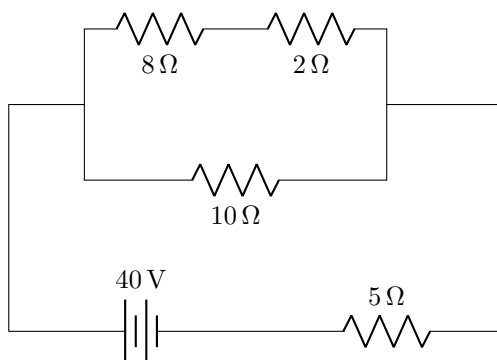3. Find the current going through the battery in the circuit below.



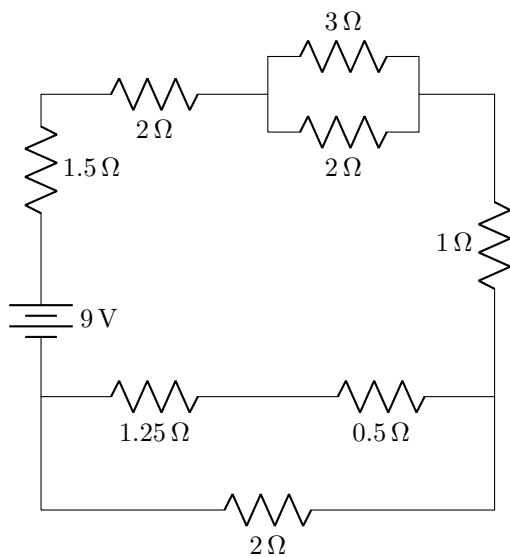4. Find the current going through the battery in the circuit below.




Answers: 3) 4.00 A 4) 1.36 A

Name: _____

Date: _____

Period: _____

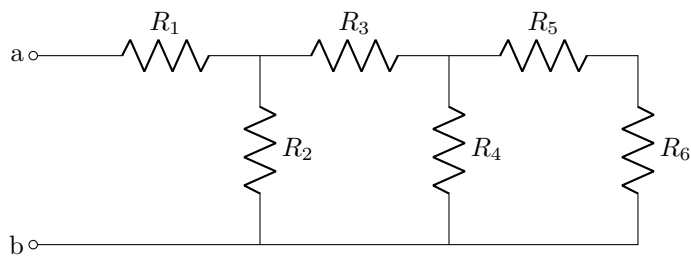5. Consider the following circuit, in which $R_1 = R_3 = R_5 = R_6 = 1\text{ k}\Omega$ and $R_2 = R_4 = 2\text{ k}\Omega$.



- (a) Calculate Equivalent Resistance
- (b) A 9-volt battery is connected between points a and b . Calculate the current through *each* resistor.
- (c) Calculate the potential difference across each resistor.

Name: _____

Date: _____

Period: _____

6. **Bonus:** Calculate the equivalent resistance of a cube that has a 1-ohm resistor along each edge.

