


Name: _____

Date: _____


Period: _____

Equivalent Resistance

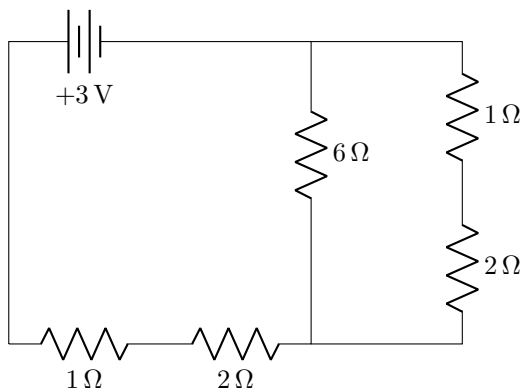1. **Consolidation:** Find the current going through the battery in the circuit below.



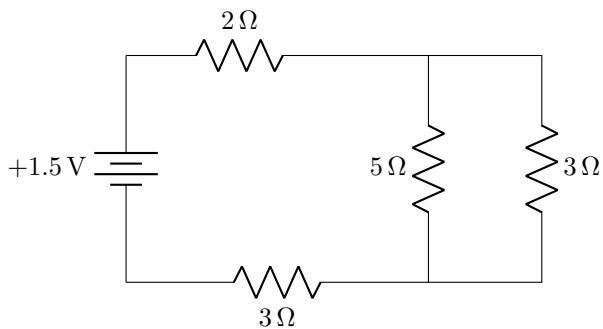2. Find the current going through the battery in the circuit below.




Name: _____

Date: _____

Period: _____

3. Consider the following circuit.

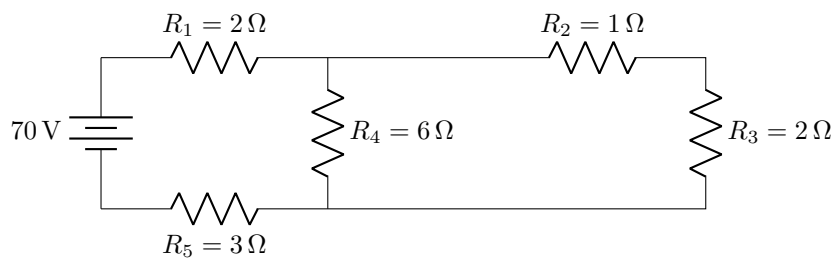

- (a) Calculate Equivalent Resistance
- (b) Calculate the current through *each* resistor.
- (c) Calculate the potential difference across each resistor.

Current I (Amperes)	Potential Difference ΔV (Volts)
Battery	
$R_1 = 2\ \Omega$	
$R_2 = 1\ \Omega$	
$R_3 = 2\ \Omega$	
$R_4 = 6\ \Omega$	
$R_5 = 3\ \Omega$	